

OPAMP (operational amplifier)





Dr. Mithun Kr. Bhowal

What is opamp?

Opamp is a high gain direct couple amplifier whose response characteristics are externally controlled by negative feedback arrangement.

Feedback? A portion of output signal of an amplifier is feedback and superimpose on the input signal.

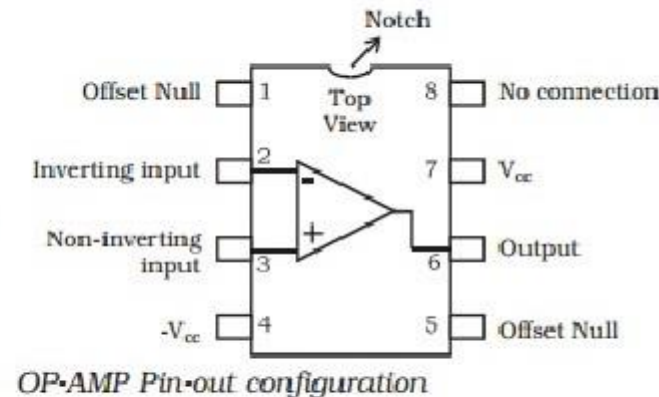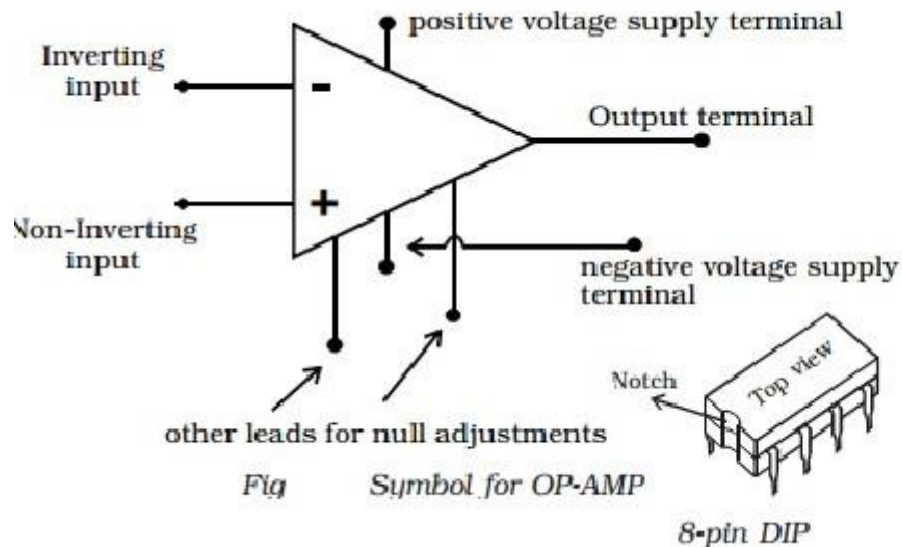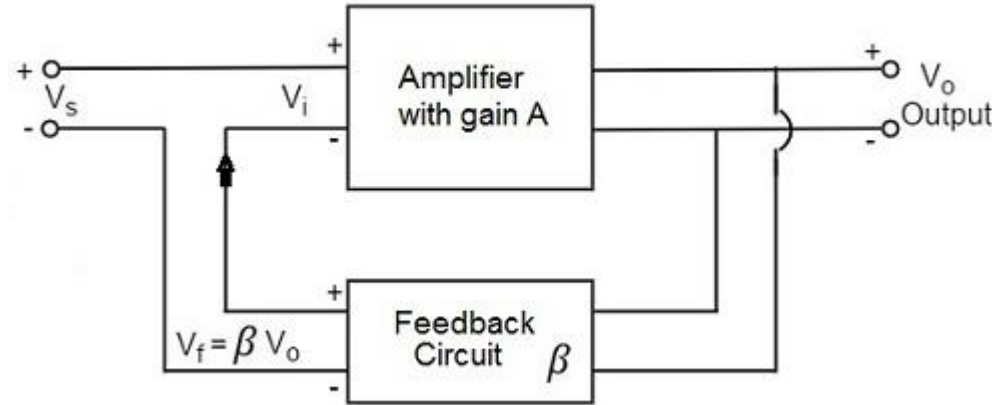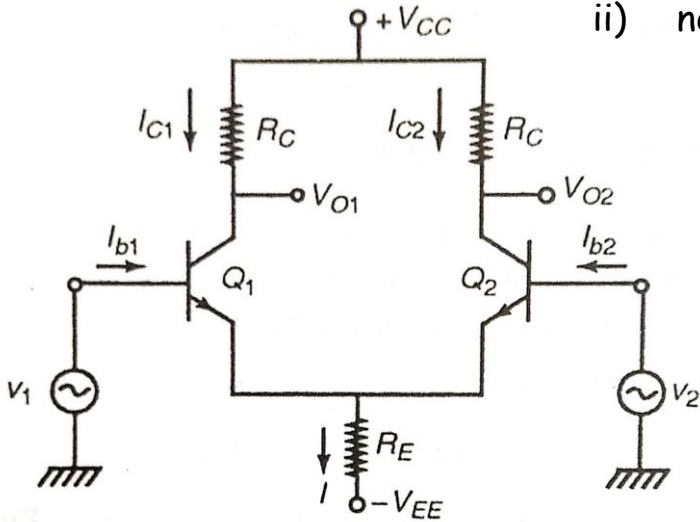- i) Positive feedback: if the feedback component adds to the i/p signal is in phase with the input signal.
- ii) negative feedback: if the feedback component subtracts to the i/p signal is in phase with the input signal.



Why "operational"?

it perform mathematical operation like addition, subtraction, integration, differentiation etc.

IC 741


Characteristics of an ideal opamp:

- i) Infinite voltage gain ($A_V = \infty$)
- ii) Infinite input resistance ($R_i = \infty$)
- iii) Zero output resistance ($R_o = 0$)
- iv) Zero output voltage when input voltage is zero
- v) Infinite bandwidth
- vi) Characteristics not drift with temperature
- vii) Infinite CMRR
- viii) Infinite slew rate

Practical opamp differ from ideal opamp:


Voltage gain 10^3 to 10^6
 Input impedance, $150\text{ K}\Omega$ to $100\text{ M}\Omega$
 o/p impedance 0.75 to $1.00\text{ }\Omega$
 BW finite, upto 100 KHz
 Practical opamp don't have perfect balance

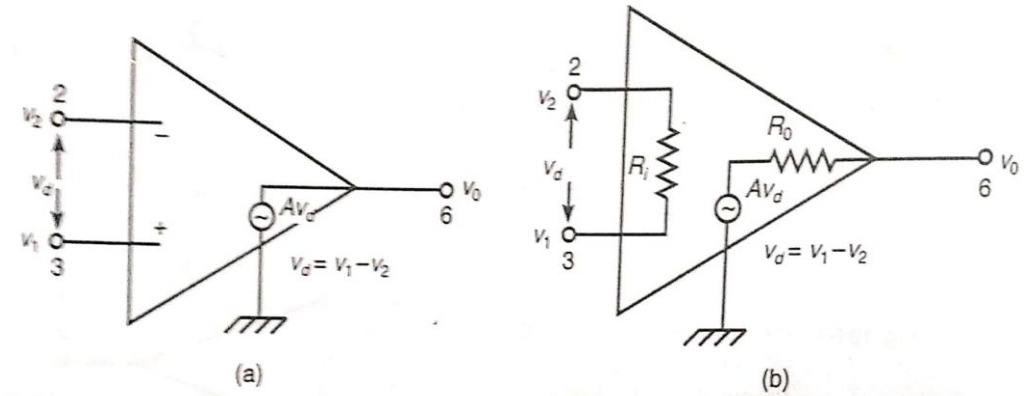A.C. equivalent circuit of a) ideal opamp b) practical opamp



CS Scanned with CamScanner

Common mode rejection ration (CMRR):

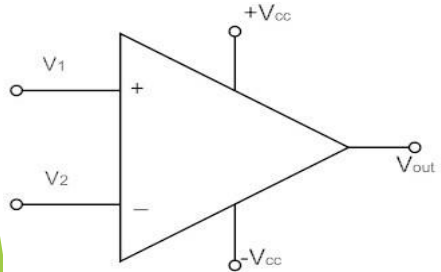

The difference of the input voltage, $V_d = V_1 - V_2$ ---(1)

Average of the input voltage, $V_C = \frac{V_1 + V_2}{2}$ ---(2)

$V_0 = A_1 V_1 + A_2 V_2$ ---(3)

Solving eq (1) and (2)

$$V_1 = V_C + \frac{V_d}{2}$$

$$V_2 = V_C - \frac{V_d}{2}$$

Putting the value of V_1 and V_2 in eq (3) we get,

$$\begin{aligned} V_0 &= A_1 \left(V_C + \frac{V_d}{2} \right) + A_2 \left(V_C - \frac{V_d}{2} \right) \\ &= \frac{1}{2} (A_1 - A_2) V_d + (A_1 + A_2) V_C \\ &= A_d V_d + A_C V_C \end{aligned}$$

Where $A_d = \frac{1}{2} (A_1 - A_2)$ = voltage gain for difference signal

$A_C = (A_1 + A_2)$ = common mode signal

CMRR is the ration between the voltage gain for difference signal and common mode signal.


$$CMRR = \left| \frac{A_d}{A_C} \right|$$

Slew rate:

Maximum rate of change of output voltage per unit of time and is expressed in volt per microsecond


$$SR = \frac{dV_0}{dt} \quad \text{v}/\mu\text{s}$$

Opamp offset null adjustment:

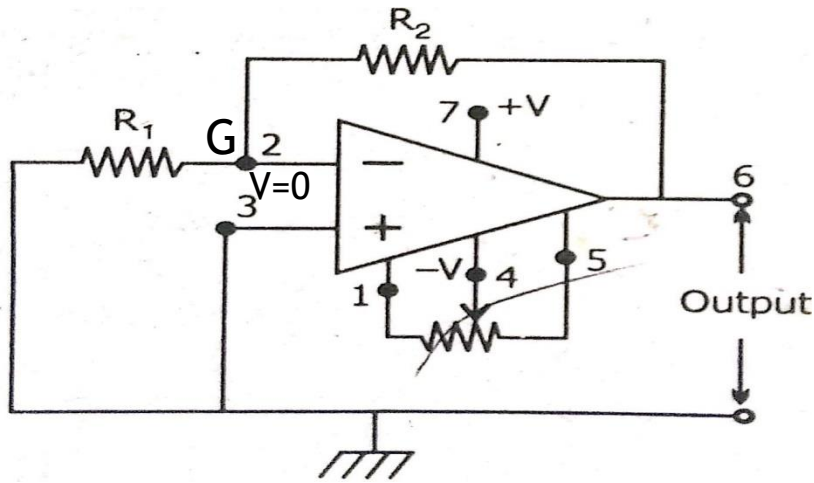


- ❑ For some application a small input offset voltage effect the output voltage. So offset null adjustment are use to minimize the effect of input offset voltage.
- ❑ 10 K Ω potentiometer are connected to the pin 1 and 5 while the wiper is connected to $-V$ dc supply.
- ❑ The potentiometer knob is adjusted to get zero output voltage.

Concept of virtual ground:

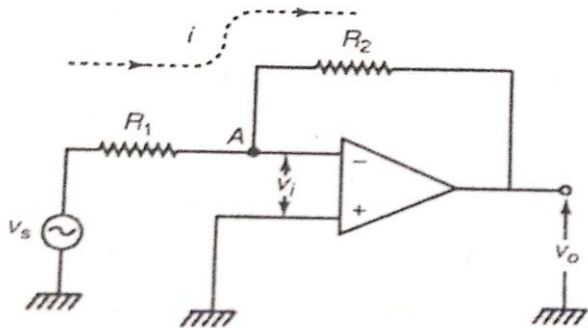

- ❑ There is a virtual ground at the point A.
- ❑ The word virtual is used to imply that through the point A is effectively connected to ground, no current actually flows into this short.
- ❑ It is not actual ground. The concept of virtual ground makes the analysis and understanding of many OPAMP circuits very simple.

Inverting amplifier:

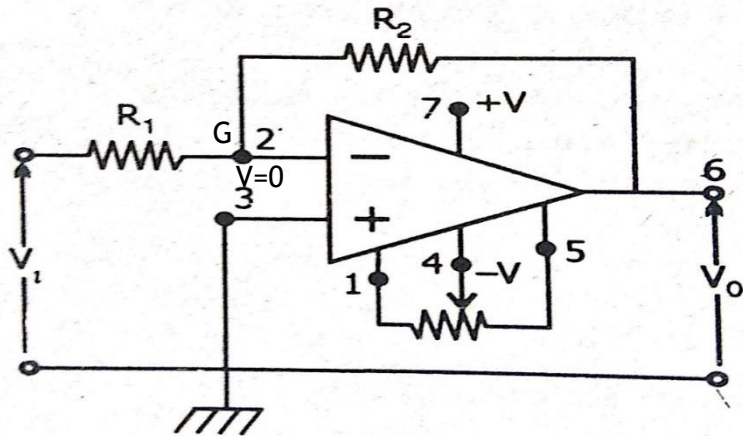

The current through R_1 is, $\frac{V_i - V}{R_1}$

The current through R_2 is, $\frac{V - V_o}{R_2}$

Due to virtual ground, $\frac{V_i - V}{R_1} = \frac{V - V_o}{R_2}$


$$\text{Or, } \frac{V_i}{R_1} = -\frac{V_o}{R_2}$$

Or, $V_o = -\frac{R_2}{R_1} V_i$, expression of o/p voltage

$$\text{Voltage gain, } A_V = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

The -ve sign signifies that the o/p voltage is inverted with respect to the input voltage.

Non-Inverting amplifier:

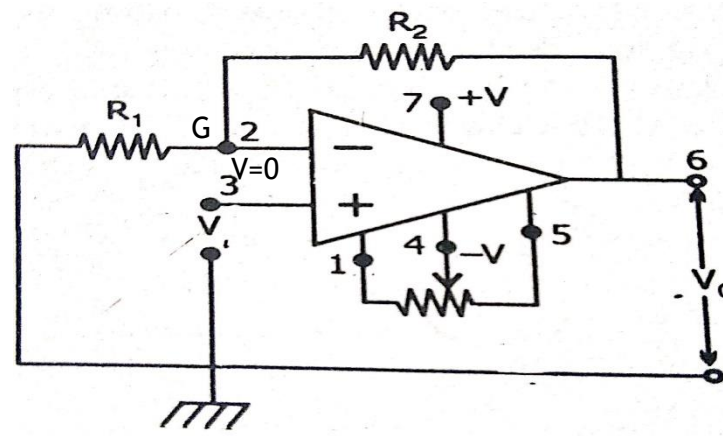

The current through R_1 is, $\frac{0 - V_i}{R_1}$

The current through R_2 is, $\frac{V_i - V_o}{R_2}$

Due to virtual ground, $\frac{-V_i}{R_1} = \frac{V_i - V_o}{R_2}$

$$\text{Or, } \frac{-V_i}{R_1} = \frac{V_i}{R_2} - \frac{V_o}{R_2}$$


$$\text{Or, } \frac{V_o}{R_2} = \frac{V_i}{R_2} + \frac{V_i}{R_1}$$

$$\text{Or, } V_o = \left(1 + \frac{R_2}{R_1}\right) V_i, \text{ expression of o/p voltage}$$

$$\text{Voltage gain, } A_V = \frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_1}\right)$$

The +ve sign signifies that there is no phase difference between input and output.

Unity gain buffer:

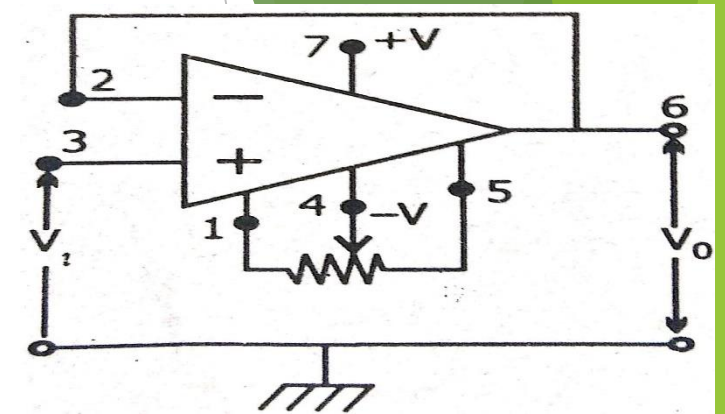

$$A_V = 1 + \frac{R_2}{R_1}$$

As $R_1 = \infty$ and $R_2 = 0$

$$A_V = 1$$

It allows the i/p voltage to be transferred to the o/p without any change.