

B.Tech. 2nd Semester Examination, 2021

BE 205: BASIC ELECTRONICS

Full Marks: 70

Time: 3 Hours


Group A (Answer any Five questions)

1. 2× 5 = 10
- a) Why does a pure semiconductor behave like an insulator at absolute zero temperature? 2
 - b) Why is Si preferred over Ge in the manufacture of semiconductor device? 2
 - c) Why the width of the base region of a transistor is kept very small compare to other regions? 2
 - d) What are the parameters that control the pinch off voltage of JFET? 2
 - e) How does the negative feedback affect the performance of an inverting amplifier? 2
 - f) What is Fermi level? 2
 - g) What is modulation index and percentage of modulation? 2
 - h) State the two De-Morgan's theorem. 2

Group B (Answer any Four questions)

2. 15×4= 60
- a) In an intrinsic Si, the fermi level lies near middle of the band gap. How does Fermi level move when it is doped with (i) Phosphorus (ii) boron atoms? 2
 - b) Can the Fermi level be pushed up into the conduction band? If yes, explain how and if not explain why? 3
 - c) Draw the energy band diagram for (i) an intrinsic (ii) an n-type and (iii) a p-type semiconductor. Indicate the positions of the fermi, the donor, and the acceptor levels. 6
 - d) Briefly explain the operation of Full wave rectifier. 4

- | | | |
|----|---|-------|
| 3. | a) Explain different components of current flowing through the structure of a N-P-N transistor | 5 |
| | b) In a CB configuration of a PNP transistor the current amplification factor is 0.988. Determine the base current if emitter current is 1.2 mA. Neglect collector leakage current. | 2 |
| | c) Explain with diagram the following regions in a transistor in CE mode
(i) Active (ii) Saturation (iii) Cutoff. | 3 |
| | d) Draw the equivalent circuit of zener diode as voltage regulator and explain. | 4 |
| | e) What is an LED? | 1 |
| 4. | a) What do you mean by Zener and Avalanche breakdown in P-N junction semiconductor diode? | 2 |
| | b) Sketch the basic structure of an N-channel JFET and draw the volt-ampere (V/I) characteristics. Explain each region in the graph. | 1+1+2 |
| | c) What is dynamic resistance of a JFET? | 2 |
| | d) Why are N-channel MOSFET preferred over P-channel ones in integrated circuit? | 2 |
| | e) What is the significant difference between the enhancement type and depletion type MOSFET? | 3 |
| | f) Explain the term 'channel' in a JFET. | 2 |
| 5. | a) What is virtual ground? | 2 |
| | b) Explain the use of an OPAMP as an integrator. | 4 |
| | c) Design a noninverting amplifier circuit that is capable of providing a voltage gain of 15. Assume ideal op-amp and resistance should not exceed 30 K Ω . | 2 |
| | d) Find the output of the following circuit. | 4 |

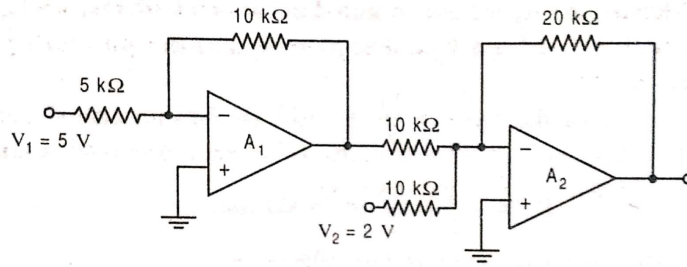

- e) State the type of number systems present in digital systems and mention their radix. 3
6. a) Simplify the following expressions:
- (i) $(\bar{A} + B + \bar{C})(\bar{A} + B + D + E)(C + D)$ 3+2
- (ii) $\bar{A}\bar{B}C + BC + AC$
- b) Using K-map deduce the simplified expression for the following function 3+1
- $$f(A,B,C,D) = \sum m(0,2,3,6,7,8,10,11,12,15)$$
- Realise the function using logic gates. 4
- c) Perform BCD addition of 974+595
- d) Convert $(10001110)_2$ to its hexadecimal equivalent. 2
7. a) Write down the truth table of a full adder. Derive the expressions for the full adder and implement the full adder using logic gates. 5
- b) What is a multiplexer? Explain the operation of a 4×1 MUX with the help of diagram. 4
- c) Draw the diagram of 3 to 8 decoder and briefly explain how it operates. 4
- d) What are sequential circuits and how do they differ from combinational circuits? Give examples of sequential circuits. 2

- | | | |
|----|---|---|
| 8. | a) What is an S-R flip flop. Draw the state table for the same. | 3 |
| | b) How is T flip flop derived from JK flip flop? Draw the diagram. | 2 |
| | c) What do you understand by signal modulation? State the types of analog modulation. | 3 |
| | d) What is frequency modulation? Derive the expression for the modulated wave in frequency modulation. | 4 |
| | e) Draw the chip diagram of a 4-bit magnitude comparator and explain with reference to this diagram how the comparator works. | 3 |