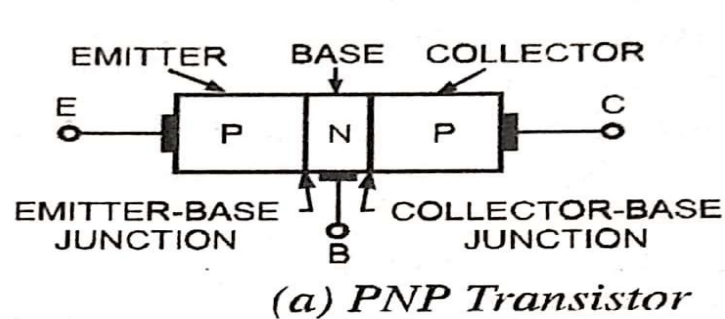


Bipolar Junction Transistor (BJT)


DR. MITHUN KR. BHOWAL
UNIVERSITY OF CALCUTTA

INTRODUCTION:


- BJT is a three layer, two junction semiconductor device.
- Two types of formation: p-n-p and n-p-n.
- Emitter, base and collector
- Each type of transistor has two junctions: emitter junction (J_E) and collector junction (J_C).



(a) PNP Transistor

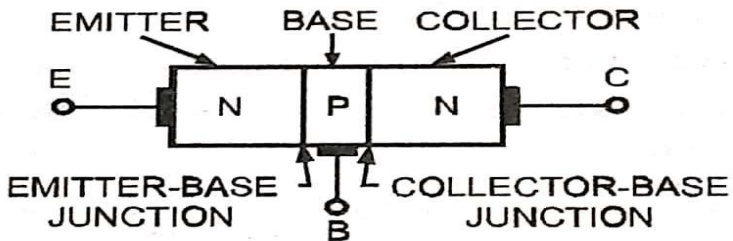


(b) NPN Transistor

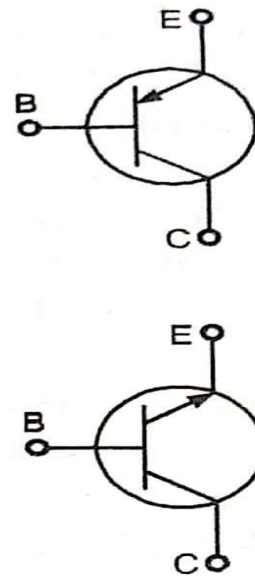

Circuit symbol

❑ Since both majority and minority carriers are involved in a junction transistor, so this device is termed the **bipolar junction device**.

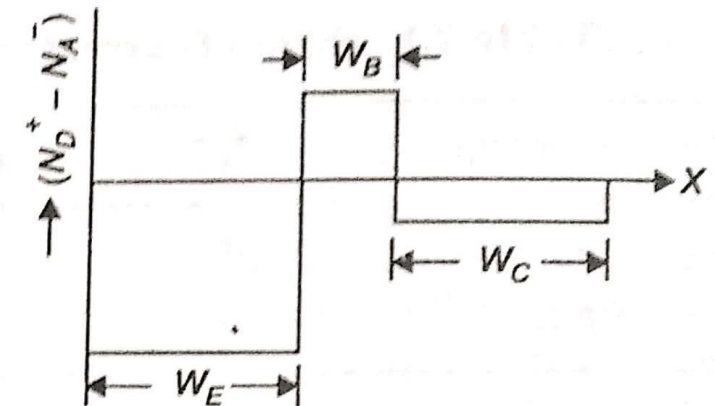
❑ Due to transistor action it is found that an almost same current passes from a low resistance input circuit to a high resistance output circuit. The term transistor has been derived from the words "transfer resistor"




CS Scanned with CamScanner
Doping profile of p-n-p transistor

❑ The doping of the emitter of a transistor is greater than of the collector. The base region is oppositely doped at a level intermediate between the emitter and the collector.

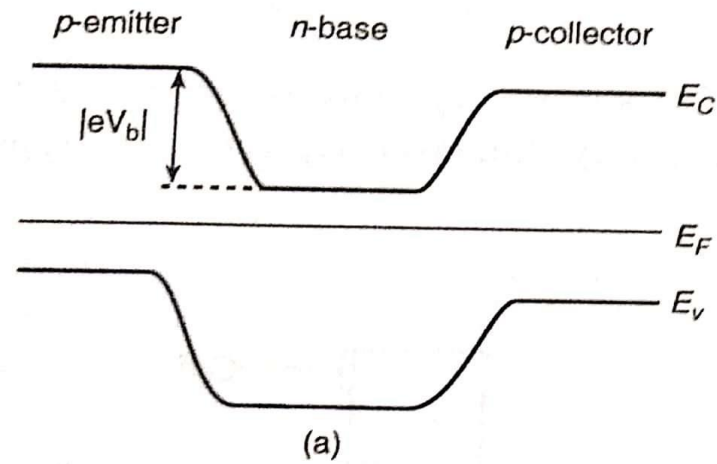Energy band diagram of a symmetric transistor:




Unbiased

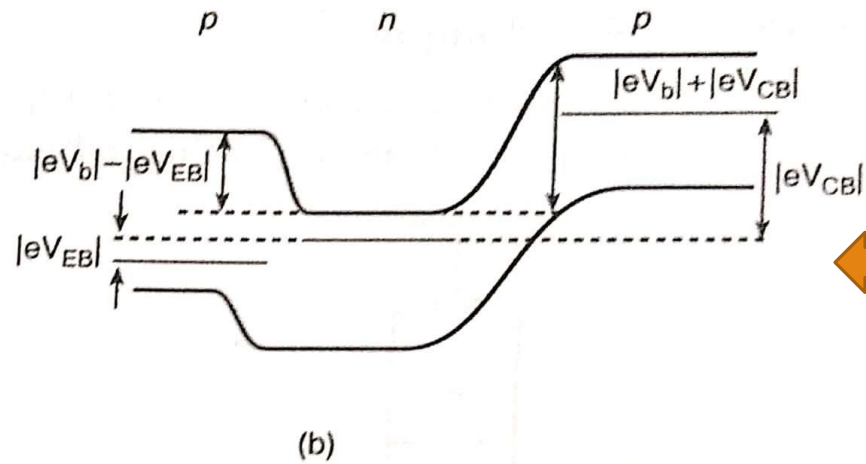


Biased

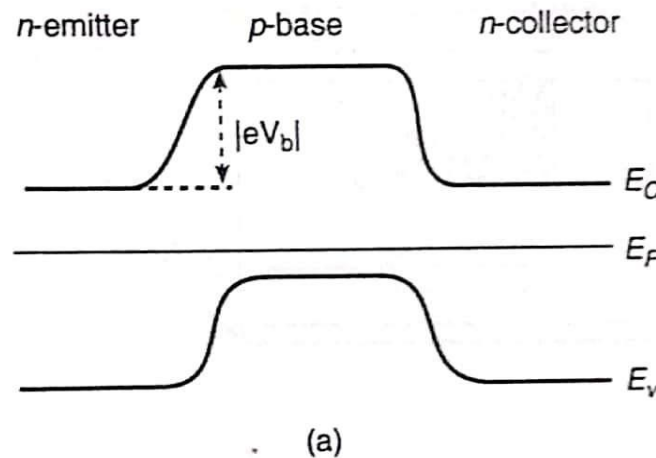Energy band diagram with E-B junction forward bias and C-B junction reverse bias.




Unbiased

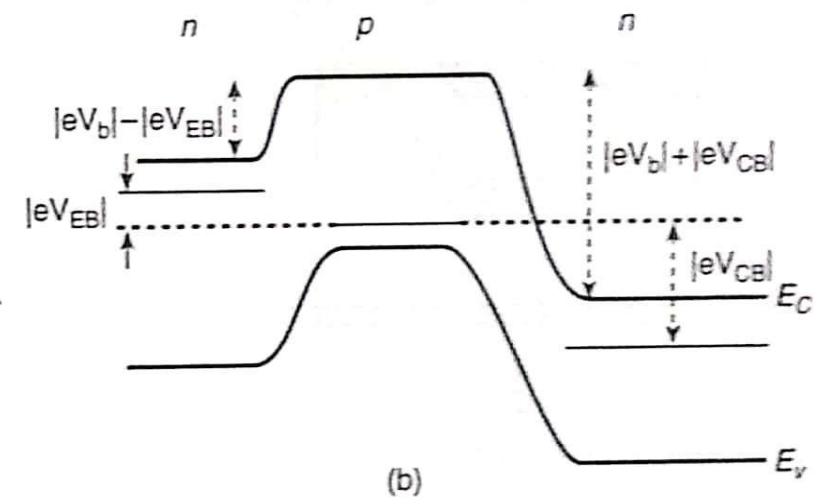


Biased

- ❑ The forward biasing of E-B junction reduce the intrinsic energy barrier eV_b to $eV_b - eV_{EB}$
- ❑ The reverse biasing of C-B junction reduce the intrinsic energy barrier eV_b to $eV_b + eV_{EB}$

Current component:

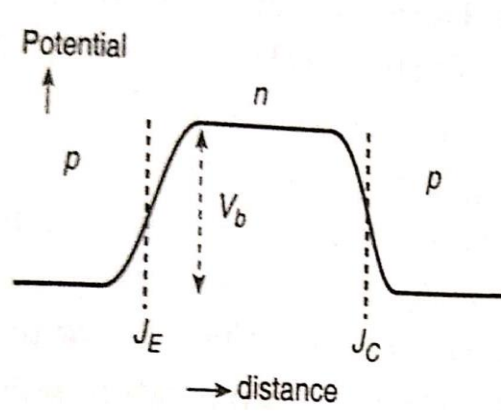


(a) Unbiased

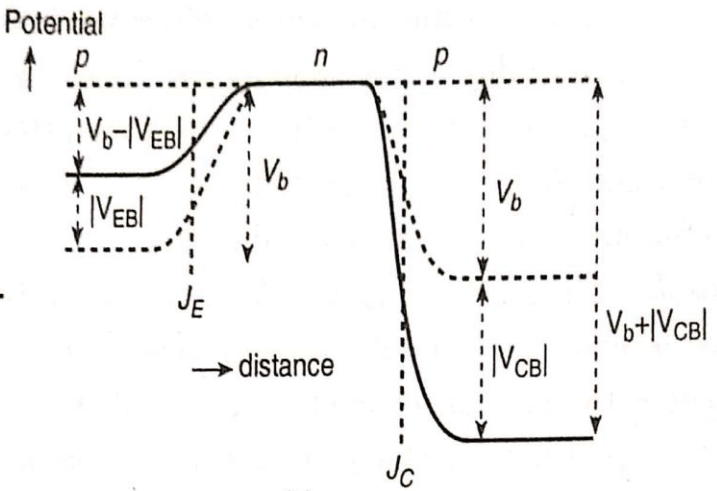

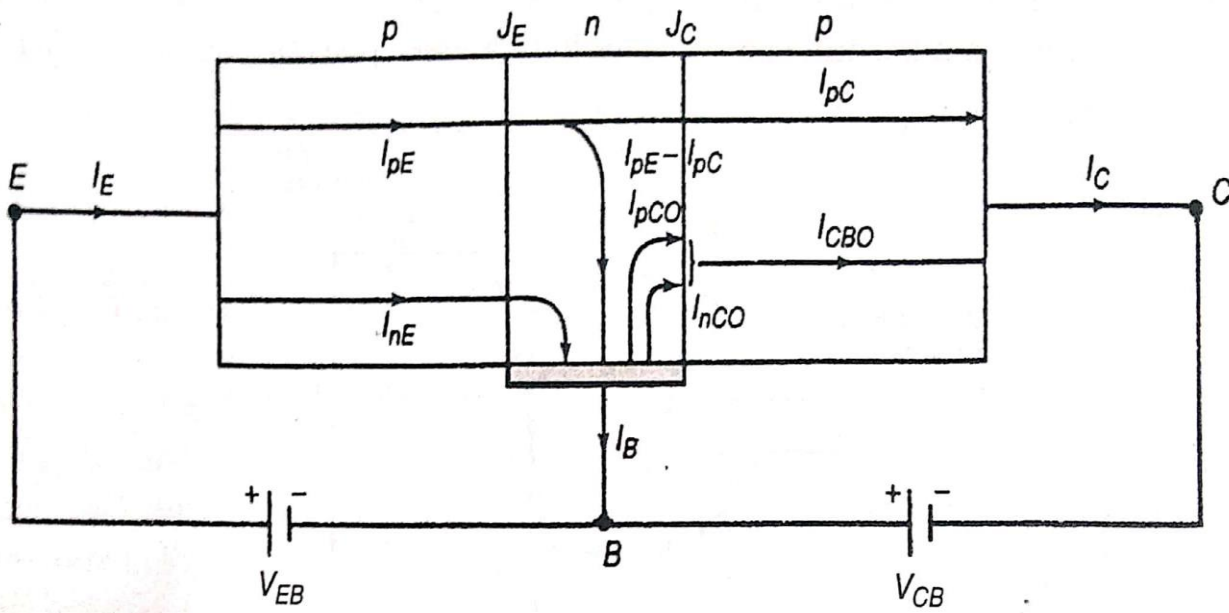
(b) Biased

Potential variation through a symmetrical p-n-p transistor



- I_{pE} = emitter current due to hole
- I_{nE} = emitter current due to electron
- Emitter current, $I_E = I_{pE} + I_{nE}$
- Base current, $I_B = I_{pE} - I_{pC}$
- I_{pC} = collector current due to hole
- I_{nCO} = current due minority carrier flowing from p-side to n-side
- I_{pCO} = current due minority carrier flowing from n-side to p-side
- Reverse collector saturation current, $I_{CO} = I_{nCO} + I_{pCO}$
- Collector current, $I_C = I_{pC} + I_{CO}$
- $I_E = I_B + I_C$

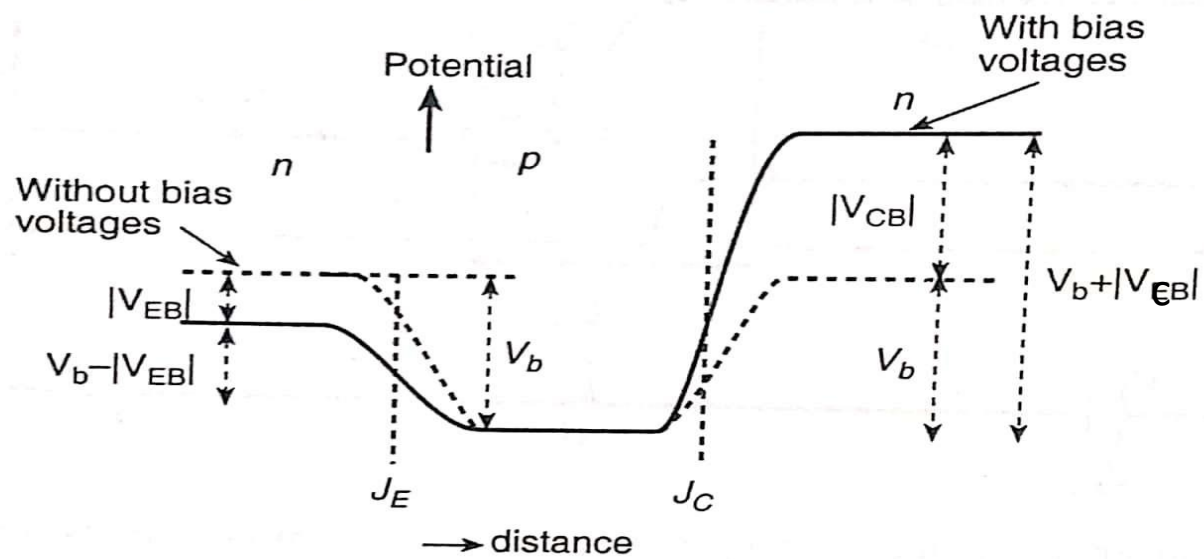Potential variation through a symmetrical n-p-n transistor



I_{nE} = emitter current due to electron

I_{pE} = emitter current due to hole

Emitter current, $I_E = I_{nE} + I_{pE}$

Base current, $I_B = I_{nE} - I_{nC}$

I_{nC} = collector current due to hole


I_{nCO} = current due minority carrier flowing from p-side to n-side

I_{pCO} = current due minority carrier flowing from n-side to p-side

Reverse collector saturation current, $I_{CO} = I_{nCO} + I_{pCO}$


Collector current, $I_C = I_{pC} + I_{CO}$

$$I_E = I_B + I_C$$

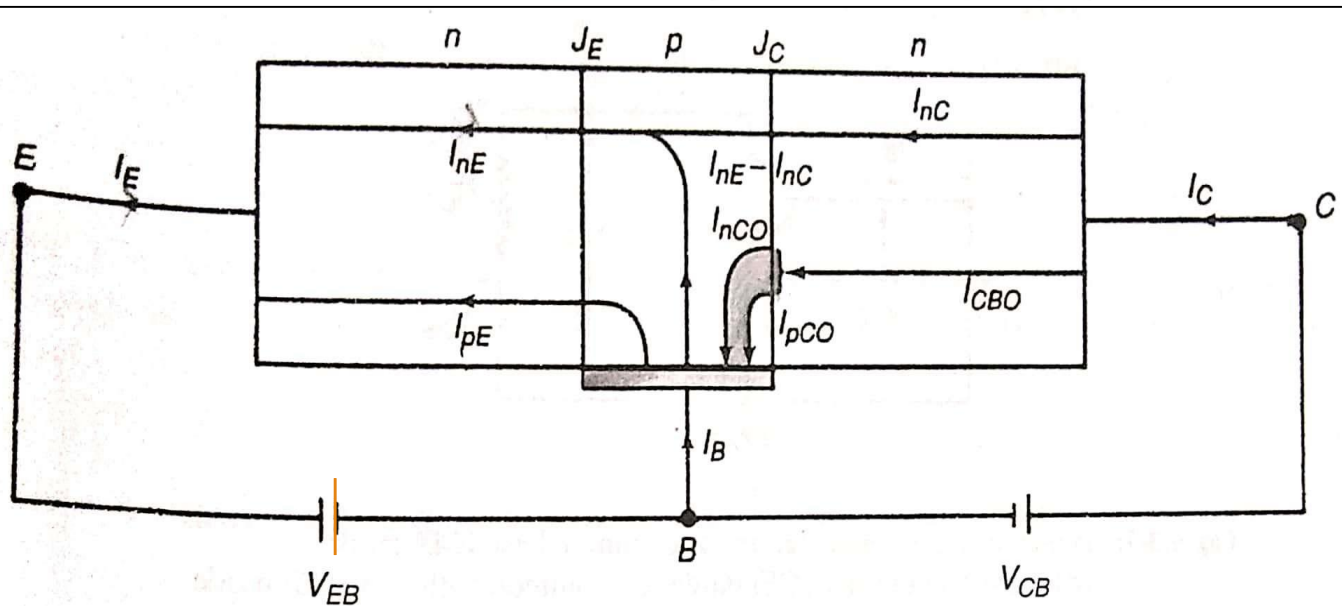


Modes of connection of a transistor:

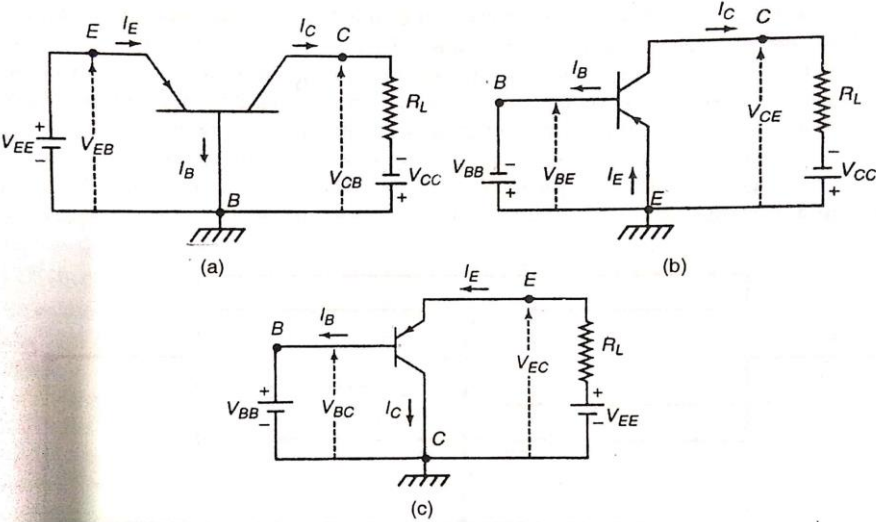- ☐ Common emitter (CE) mode
- ☐ Common base (CB) mode
- ☐ Common collector (CC) mode



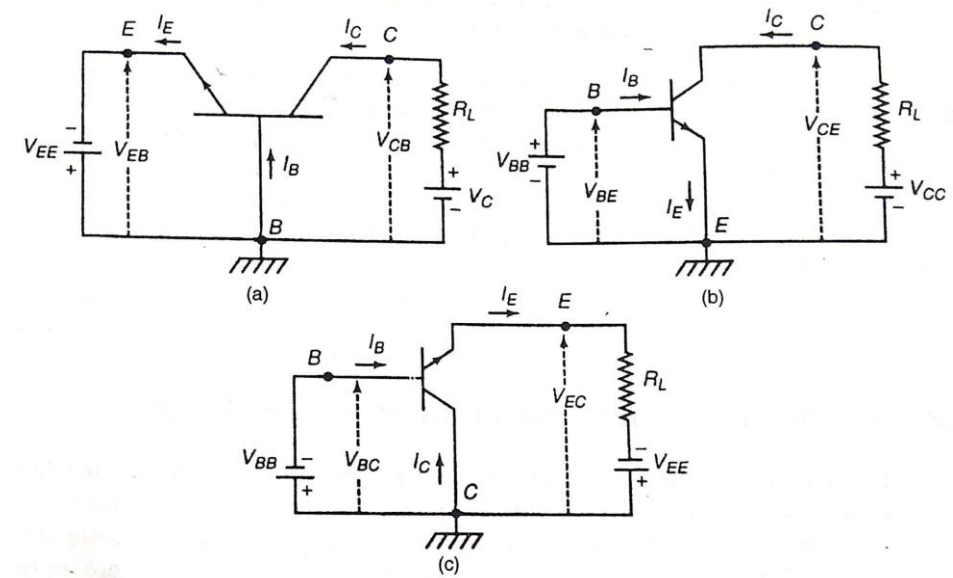p-n-p transistor connected in (a) CB (b) CE (c) CC mode



n-p-n transistor connected in (a) CB (b) CE (c) CC mode

Transistor α and β :

α represent the fraction of emitter current that can injected into the base and reach the collector. α is called dc current gain of the common base transistor. α lies between 0.95 to 0.995

$$\alpha = \frac{I_C}{I_E}$$

The maximum current gain of a transistor operated in the common-emitter mode is denoted by the parameter β . It is also denoted by h_{FE} . Commercial transistor have values of h_{FE} in the range from 20 to 200

$$\beta = \frac{I_C}{I_B}$$

Relation between α and β :

We know, $I_E = I_B + I_C$





$$\Rightarrow \frac{I_E}{I_C} = \frac{I_B}{I_C} + 1$$

$$\Rightarrow \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\Rightarrow \alpha = \frac{\beta}{1 + \beta}$$

$$\Rightarrow \beta = \frac{\alpha}{1 - \alpha}$$




Common base characteristics:

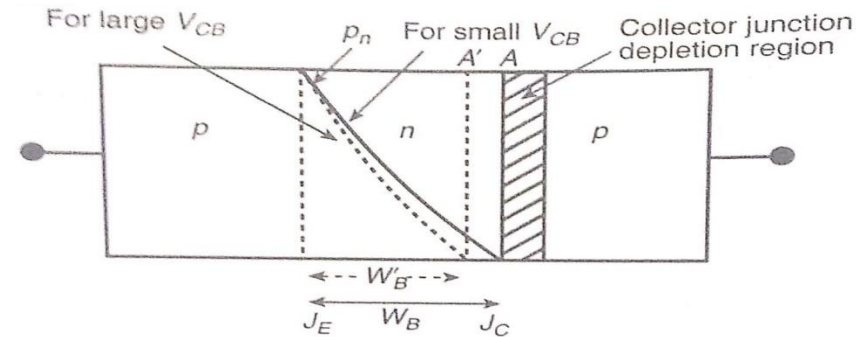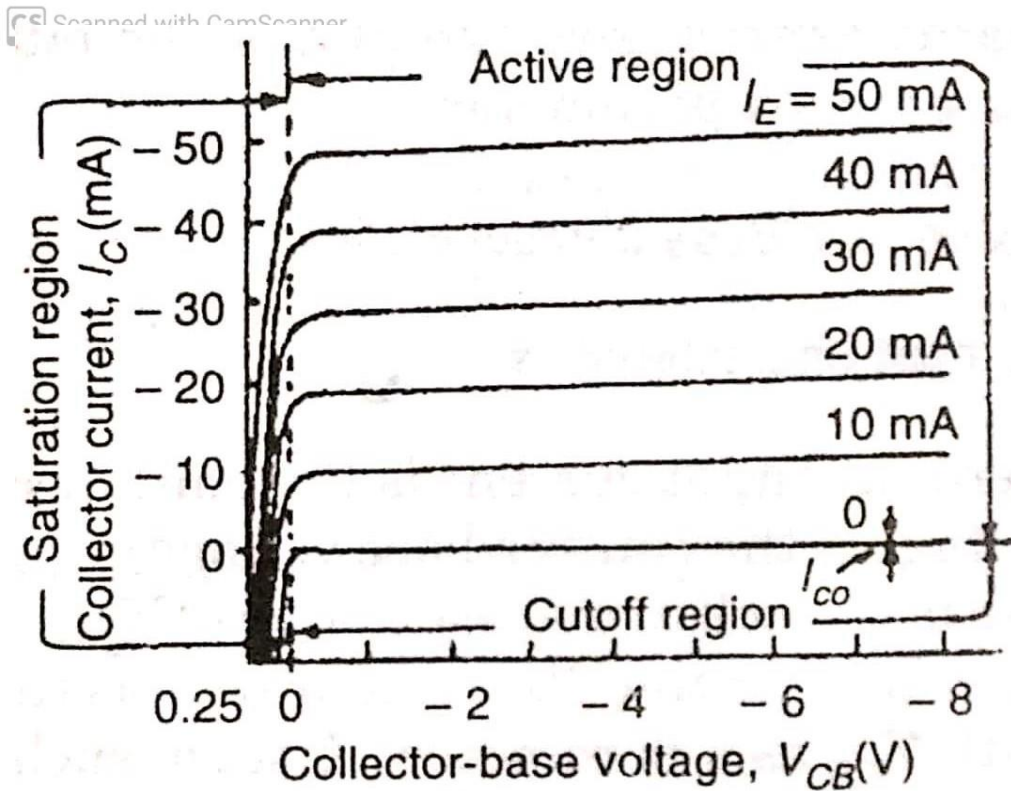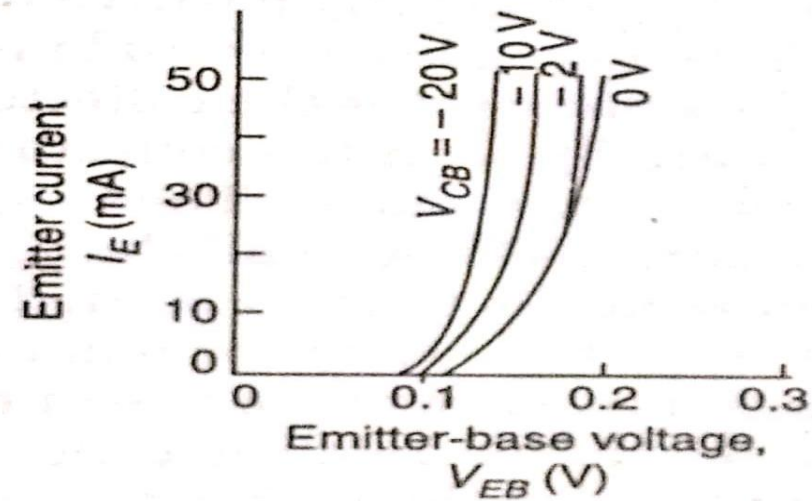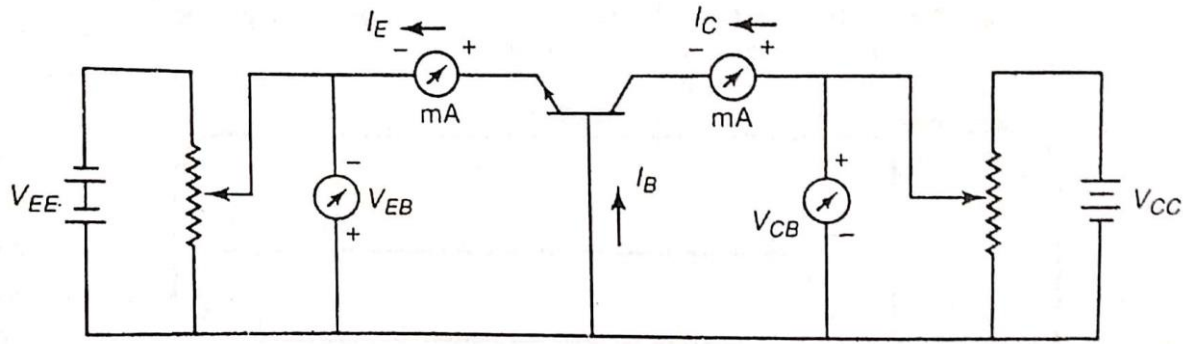

When V_{CB} increases, the width of the depletion region at the collector-Base junction increases, thereby reducing the effective base width. The change of the effective base width by the collector voltage is termed the **Early effect or base width modulation.

** punch through: at a certain reverse voltage of the J_C , reducing the effective base width to zero.

Common emitter characteristics:

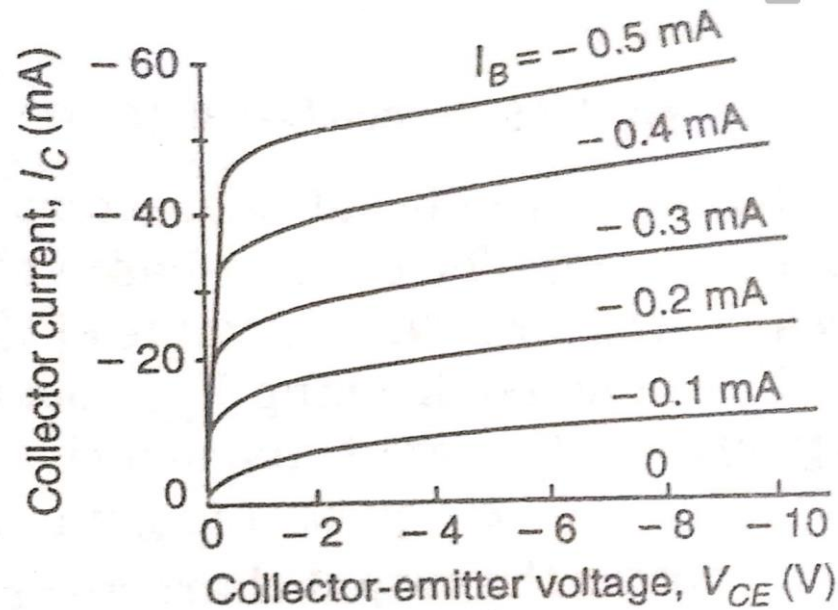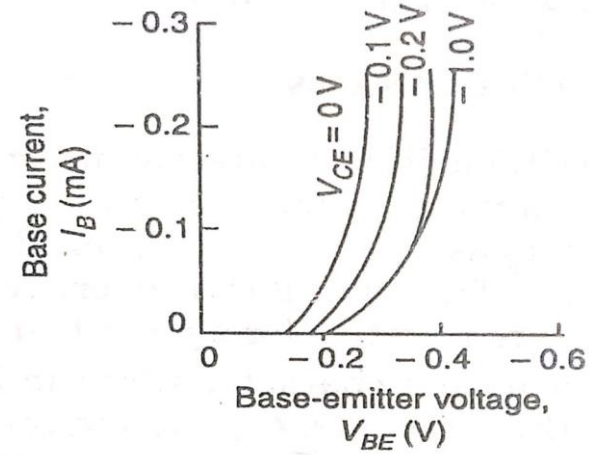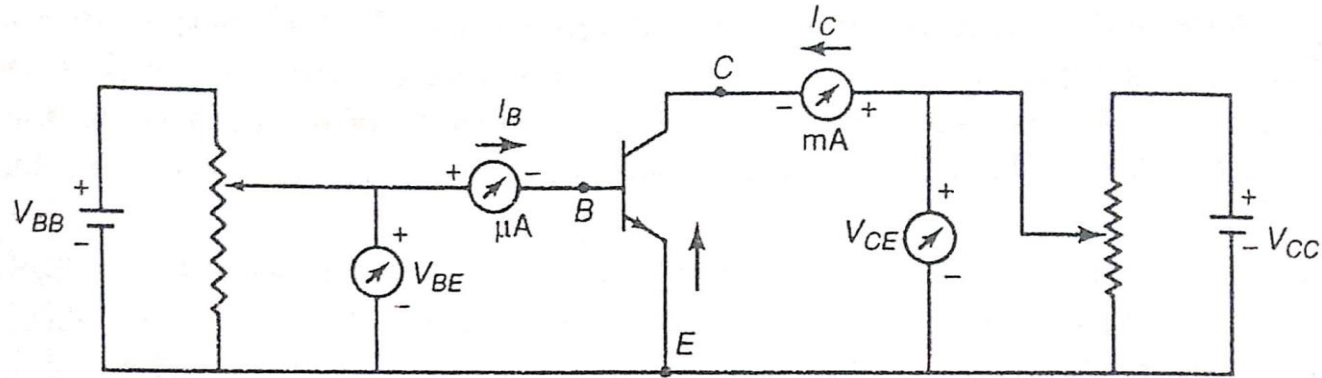

Thank you